
2024 Digital IC Design

Homework 3: matrix multiplier

NAME									
Student ID		P76124265							
Simulation Result									
Functional simulation	Score: 100		Gate-level simulation	Score:	Clock	25.0(ns)	Gate-level simulation tim	e 137550 simulation time (ns)	
your pre-sim result of test patterns Fattern 3 pass									
						453 / 55,856 (< 1 %)			
Total memory bit						0 / 2,396,160 (0 %)			
Embedded multiplier 9-bit element						1/308 (< 1 %)			
your flow summary									
Flow Summary <= < < Filter>> Flow Status Summary Quartus Prime Version 20. Revision Name MM Top-level Entity Name MM Family Cyc Device EPA Timing Models Fin Total logic elements 45: Total registers 310 Total pins 36 Total virtual pins 0 Total memory bits 0 / Embedded Multiplier 9-bit elements 11/						uccessful - Wed May 08 14:47:25 2024 0.1.1 Build 720 11/11/2020 SJ Lite Edition MM MM yclone IV E P4CE55F23A7 inal 53 / 55,856 (< 1 %) 10 6 / 325 (11 %)			
Description of your design									

MM 架構如下:

 - State register: 循序電路,存 next stage 模組產生的 state
- Next stage: 組合電路,根據 input 和目前的 state 決定下一個 state
- Output logic: 循序電路,根據 state 決定 output
- Datapath: 循序電路,根據 state 和 input 進行運算



Load 完 mat1 和 mat2,如果 mat1 和 mat2 無法相乘,就進到 Illegal; 否則就到 MAT_MUL, MAT_MUL 將一個 row 乘一個 col 拆成 MAT1_COL 個 clock 完成,即每個 clock 只做一次乘法。

 $Scoring = (Total\ logic\ elements + total\ memory\ bit + 9*embedded\ multiplier\ 9-bit\ element) \times (Total\ cycle\ used*clock\ width)$